
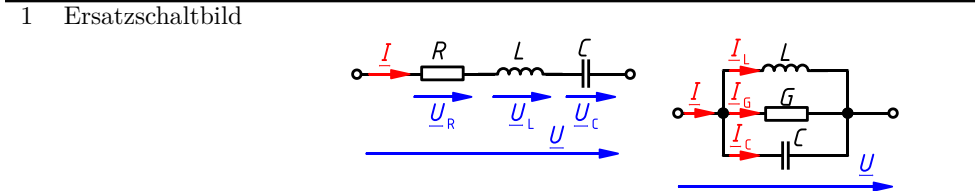


Zeile	Elementarer Reihenschwingkreis	Elementarer Parallelschwingkreis
-------	-----------------------------------	-------------------------------------

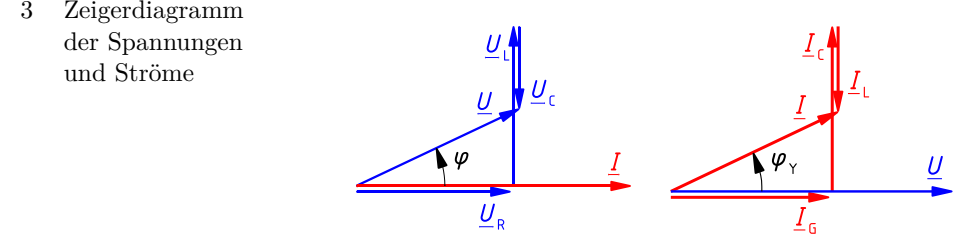

2 Klemmenverhalten	$\underline{U} = \underline{I}(R + j\omega L + \frac{1}{j\omega C})$	$\underline{I} = \underline{U}(G + j\omega C + \frac{1}{j\omega L})$
--------------------	--	--



4 Kenngrößen	$Z_0 = \sqrt{\frac{L}{C}}$	$\omega_0 = 1/\sqrt{LC}$	$Y_0 = \sqrt{\frac{C}{L}}$
--------------	----------------------------	--------------------------	----------------------------

